

Assignment 4 Report

Name: Adarsh Sinha

Stream: Electronic Systems

Roll No: 21307r005

Dept.: Electrical Engineering

Contents of the folder:

1. **assignment-4.pdf:** A copy of Assignment-4 Questionnaire
2. **Proj_Brent32:** The main quartus prime project folder.
3. **Proj_Brent32/Ety_BrentKung32.vhd:** VHDL file for Brent-Kung 32 bit adder.
4. **Proj_Brent32/Ety_Testbench.vhd:** VHDL file for Testbench
5. **Proj_Brent32/TestData.txt:** Contains the data input and reference result for the test bench. It is in a format more convenient for program to read.
6. **Proj_Brent32/TestData_separateVisible.txt:** Contains the data input and results for the test bench. It is in a format more readable for programmer.
7. **Results:** Snapshot of Results obtained
8. **Vlsi Assig4CodeExplanation.mp4:** Video explanation of the code

Task: Make 32-bit Brent-Kung Adder

Theory and reference formulae:

- 1st Order formula for carry: $C_{i+1} = G_i + P_i \cdot C_i$
- 2nd Order formula for carry: $C_{2i+2} = G_{2i+1,2i}^2 + P_{2i+1,2i}^2 \cdot C_{2i}$
- 3rd Order formula for carry: $C_{4i+4} = G_{4i+3,4i}^3 + P_{4i+3,4i}^2 \cdot C_{4i}$
- 4th Order formula for carry: $C_{8i+8} = G_{8i+7,8i}^4 + P_{8i+7,8i}^4 \cdot C_{8i}$
- 5th Order formula for carry: $C_{16i+16} = G_{16i+15,16i}^5 + P_{16i+15,16i}^5 \cdot C_{16i}$
- 6th Order formula for carry: $C_{32i+32} = G_{32i+31,32i}^6 + P_{32i+31,32i}^6 \cdot C_{32i}$

Using the Above mentioned reference formulae we can divide the Carries into following groups:

- Each Group is made based on when in the time, the variables needed to calculate these carries are available.
 - Group 1: $C_1, C_2, C_4, C_8, C_{16}, C_{32}$.
 - Group 2: $C_3, C_5, C_6, C_9, C_{10}, C_{12}, C_{17}, C_{18}, C_{20}, C_{24}$.
 - Group 3: $C_7, C_{11}, C_{13}, C_{14}, C_{19}, C_{21}, C_{22}, C_{25}, C_{26}, C_{28}$.
 - Group 4: $C_{15}, C_{23}, C_{27}, C_{29}, C_{30}$.

- Group 5: C_{31}

RTL View of the adder:

 


Figure 1: Zoomed out RTL view of the synthesised Brent-Kung 32 bit adder

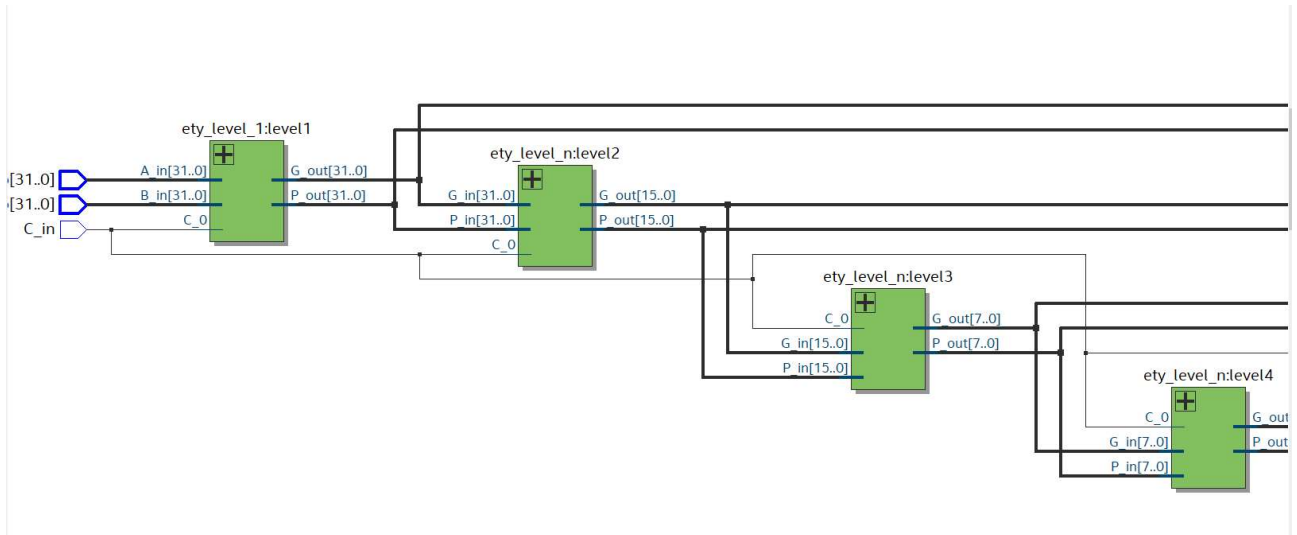


Figure 2: Encapsulated Levels of the Brunt-Kung Adder

Testbench input data arrangement

C:\Users\adars\Desktop\UnSorted\Ongoing_Work_Docs\IIT_B_CourseDocs\EE721_HDL\QuartusPrimeProjects\Proj8_VLSI_BrentKung32\TestData_separateVisible.txt ...

File Edit Search View Encoding Language Settings Tools Macro Run Plugins Window ?

temp.c main.c TestData_separateVisible.txt

1	10111010010001110000110100110101	10010101001101101001000010100101	1	10100111101111101100110111011011
2	10001101001100011101000100111101	10010001111010001100000110110110	0	100011111000110101001001011110011
3	01000100100110111000100101101100	11100100101010010101110110110101	1	100101001010001001110011100100010
4	00100010111100001011000000111101	00011110100010110101100000000011	0	001000001011111000000100001000000
5	00000100000000011111000100000010	11000100100010000111110110011001	1	011001000100010100110111010011100
6	01010010001010011000111011110100	10011011100111111001001100111101	0	011101101110010010010001000110001
7	00011001010100110111010110110000	10101100101000100111011100110000	1	01100010111110101110110011100001
8	01010011000100000010001101010101	0100111101110110111001010011100	0	01010001010001011100101011110001
9	1111100110001111001111101110111	10111100000000101011100011111011	1	110110101100100011111100001110011
10	01001100101111010100100111011110	10000010001110111010100100110000	0	011001110111110001111001100001110

Figure 3: Input and Reference results for Brunt-Kung Adder

- The First Column is the 32 bit input-A for the adder
- The Second Column is the 32 bit input-B for the adder
- The Third Column is the 1 bit input-Carry for the adder
- The Fourth Column is the 33 bit reference output for input-A + input-B + input-Carry
- There are 64 data points randomly generated contained in the file.

The Adder passes all the test inputs provided indicating proper functioning. Following are the results of the ModelSim Simulation

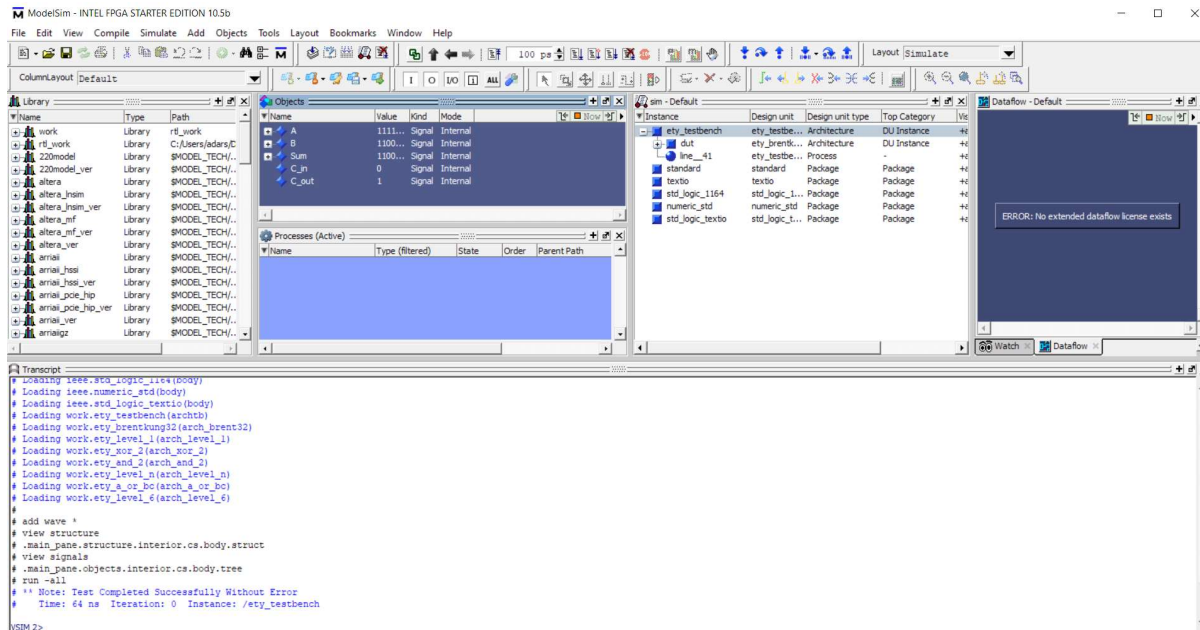


Figure 4: ModelSim View

Proof of successful completion of testbench:

```
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
# ** Note: Test Completed Successfully Without Error
# Time: 64 ns Iteration: 0 Instance: /ety_testbench
VSIM 2>
```

Figure 5: ModelSim Test Completion

Wave View of the result:

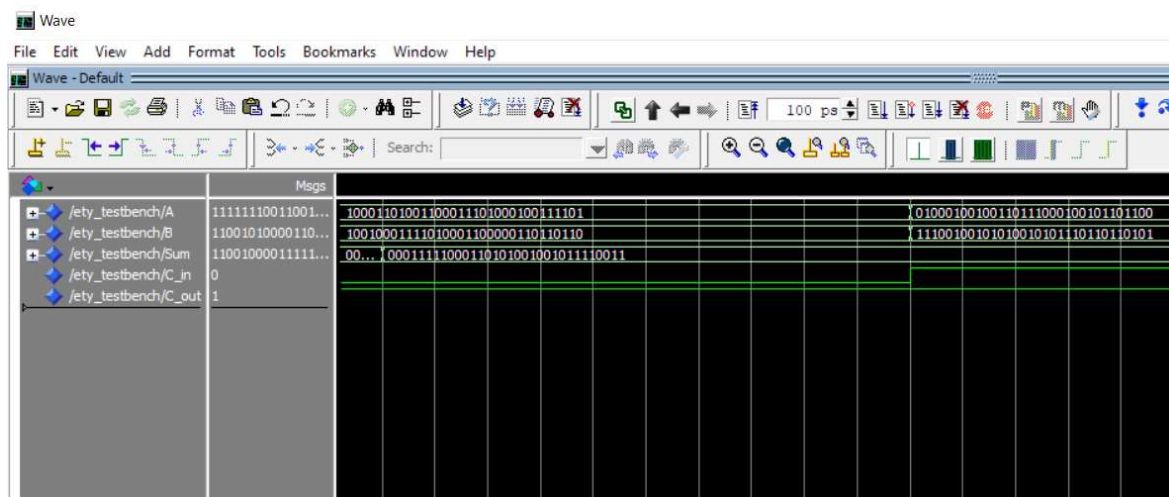


Figure 6: ModelSim Wave View

Observations:

- The Brent-Kung adder took 800 Pico Seconds to calculate One 32 bit sum, where each logic block takes 100 Pico Seconds of Delay. Therefore for 6 stages we should get around 600 picoseconds and some additional delay because the sum is generated after the carry is calculated.
- The Adder trades hardware resources for speed.